
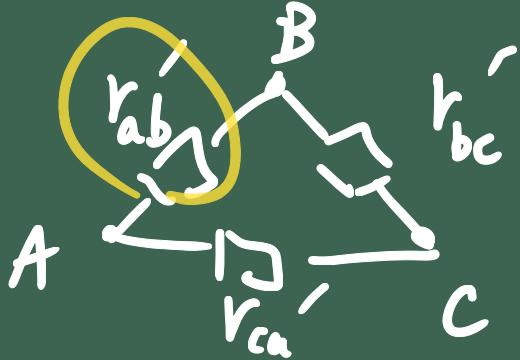


# H14 問11

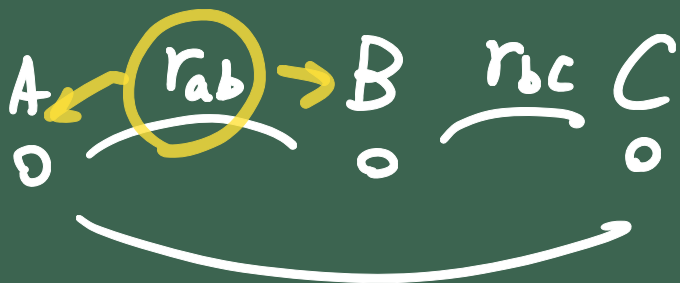

$$r_{ab} = \frac{r_{ab}' (r_{bc}' + r_{ca}')}{r_{ab}' + (r_{bc}' + r_{ca}')} = 6.6$$

$$\left. \begin{aligned} r_{ab} &= R_A + R_B = 6.6 \\ r_{bc} &= R_B + R_C = 6.0 \\ r_{ca} &= R_C + R_A = 5.2 \end{aligned} \right\} +$$

$$2(R_A + R_B + R_C) = \cancel{17.2}^{17.8}$$

$$R_A + R_B + R_C = \cancel{8.6}^{8.9}$$

$$R_B + R_C = 6.0 \quad (-)$$

$$R_A = 2.9 \text{ } (\Omega)$$

$$\cancel{R_A} + R_B + \cancel{R_C} = 8.9$$



$$\cancel{R_A} + \cancel{R_C} = 5.2 \quad (-)$$

$$R_B = 3.7 \text{ } (\Omega)$$

$$\cancel{R_A} + \cancel{R_B} + R_C = 8.9$$



$$\cancel{R_A} + \cancel{R_B} = 6.6 \quad (-)$$



$$R_C = 2.3 \text{ } (\Omega)$$

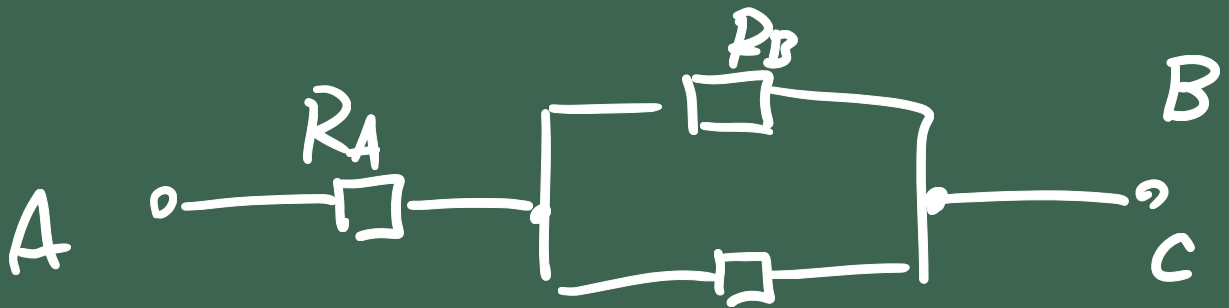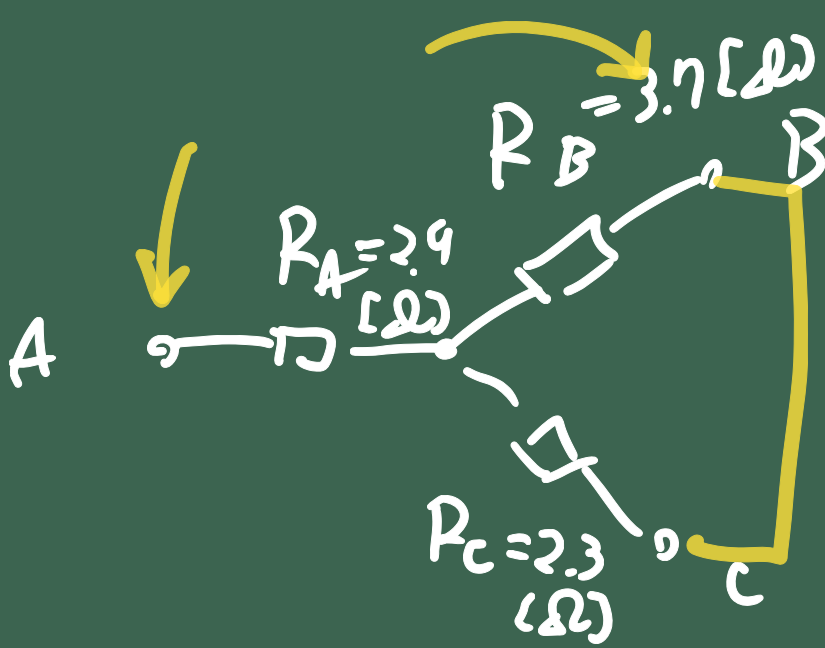

$$R_A + \frac{R_B R_C}{R_B + R_C} = 2.9 + \frac{3.7 \times 2.3}{3.7 + 2.3} = 4.3 \text{ [}\Omega\text{]}$$

H17 周5

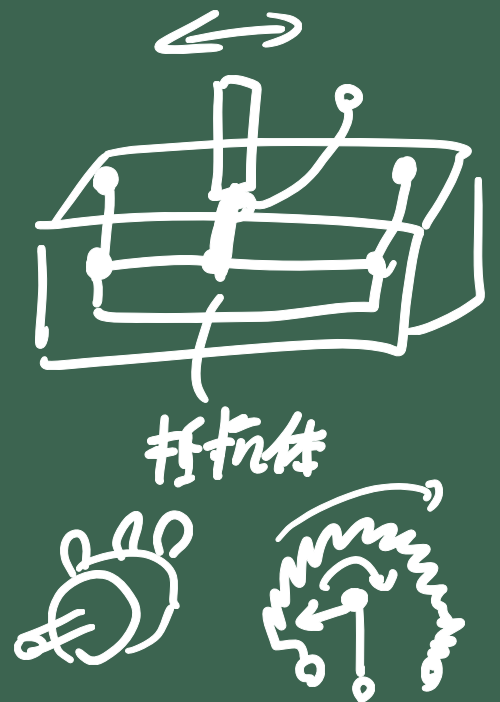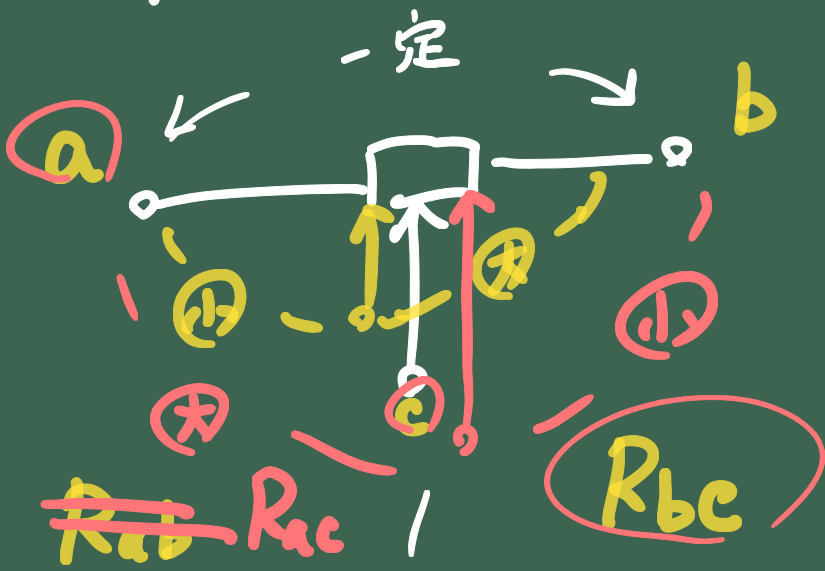

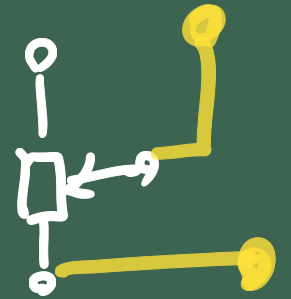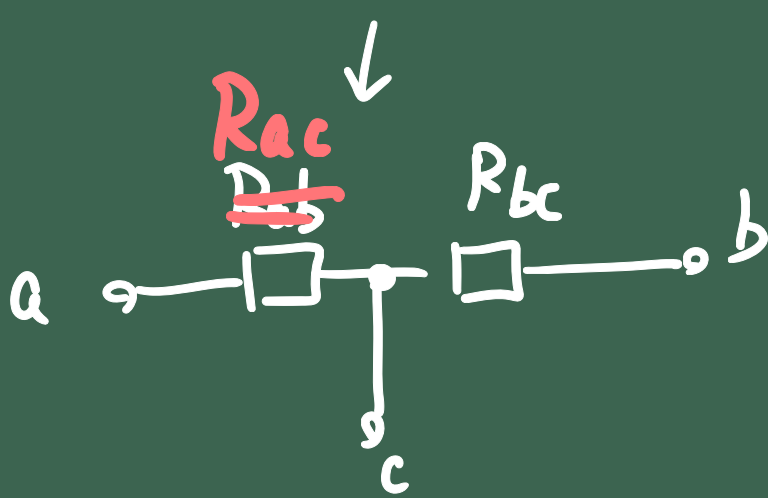

$$R_1 = 10 \Omega$$


$$I_1 = 3A$$

$$R_{ob} = 140 \Omega$$

$$R_{bc} = 140 - R_{ac}$$

$$R_2 = 5 \Omega$$

$$I = 9A$$

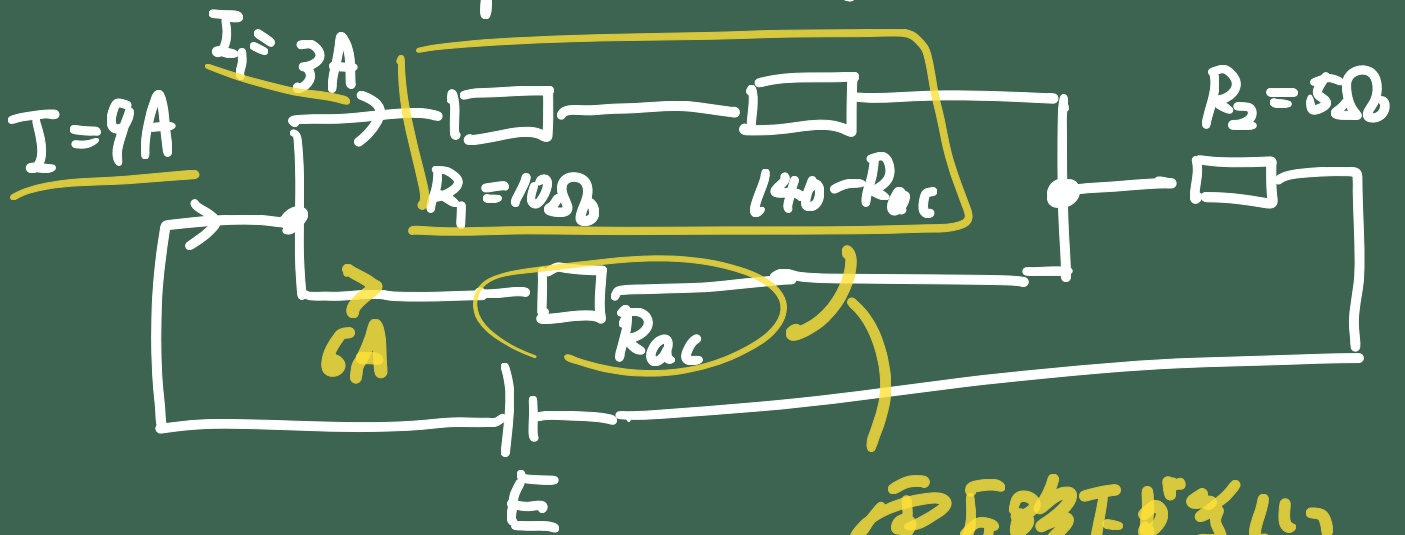

電圧降下が大きい

$$\cancel{3} \cdot (10 + 140 - R_{ac}) = \cancel{6} R_{ac}$$


$$150 - R_{ac} = 2R_{ac}$$

$$3R_{ac} = 150 \rightarrow R_{ac} = 50 \Omega$$

$$R_{bc} = 140 - R_{ac} = 140 - 50 = 90 \text{ } [\Omega]$$

$$R_{ac} : R_{bc} = 50 : 90 = 5 : 9$$

H/18 10/16

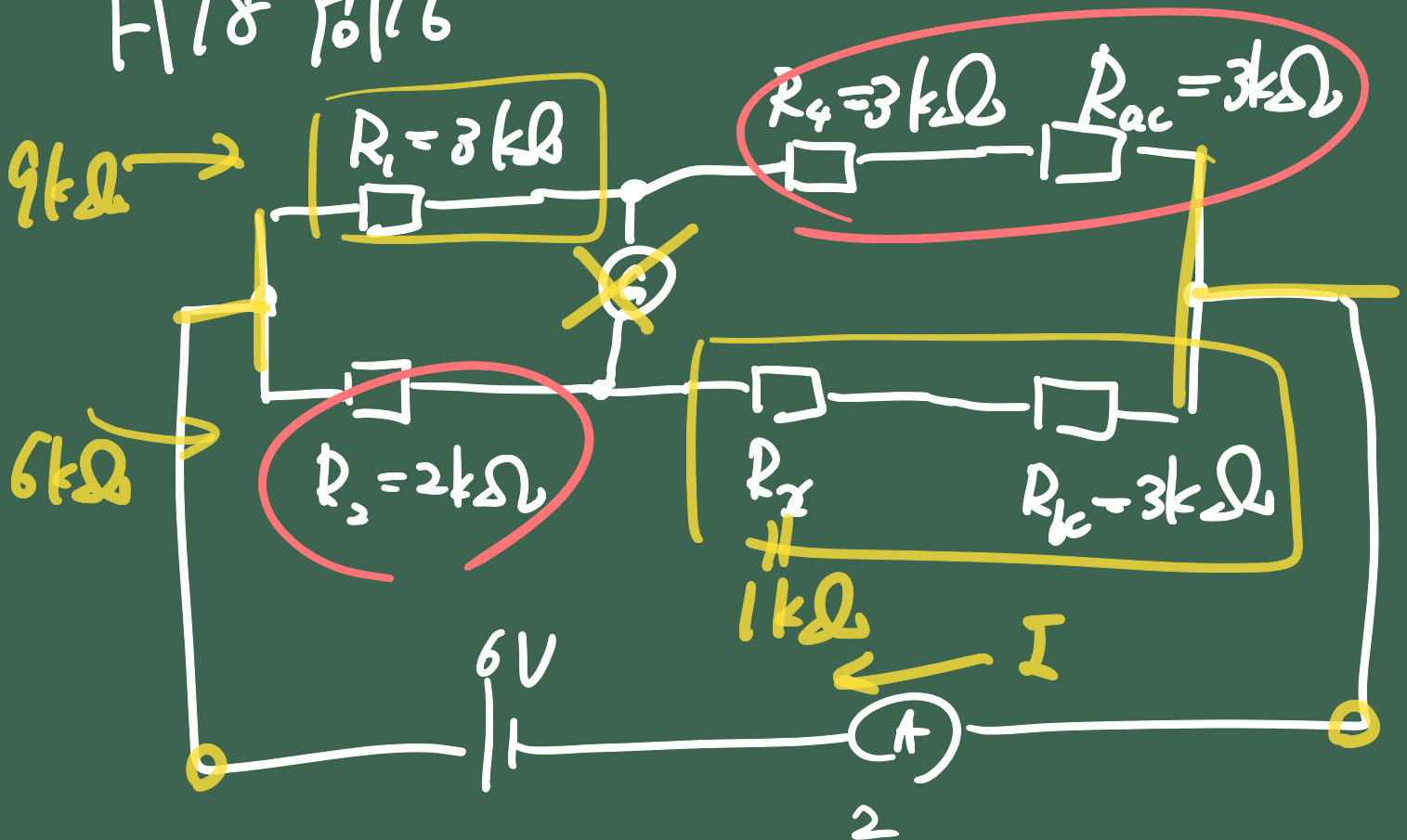

$$3 \cdot (R_x + 3) = 2 \cdot (3 + 3)$$

$$R_x + 3 = 4$$

$$\rightarrow R_x = 1 \text{ } [k\Omega]$$


合成电阻  $\frac{6 \cdot 9}{6+9} = \frac{6 \cdot 9}{15} \text{ } k\Omega$

$$\frac{15}{9} = \frac{5}{3}$$

$$I = \frac{6V}{(6 \cdot 9 / 15)k\Omega} = 1.66 \dots \text{ } mA$$



H19 10/16

(b)

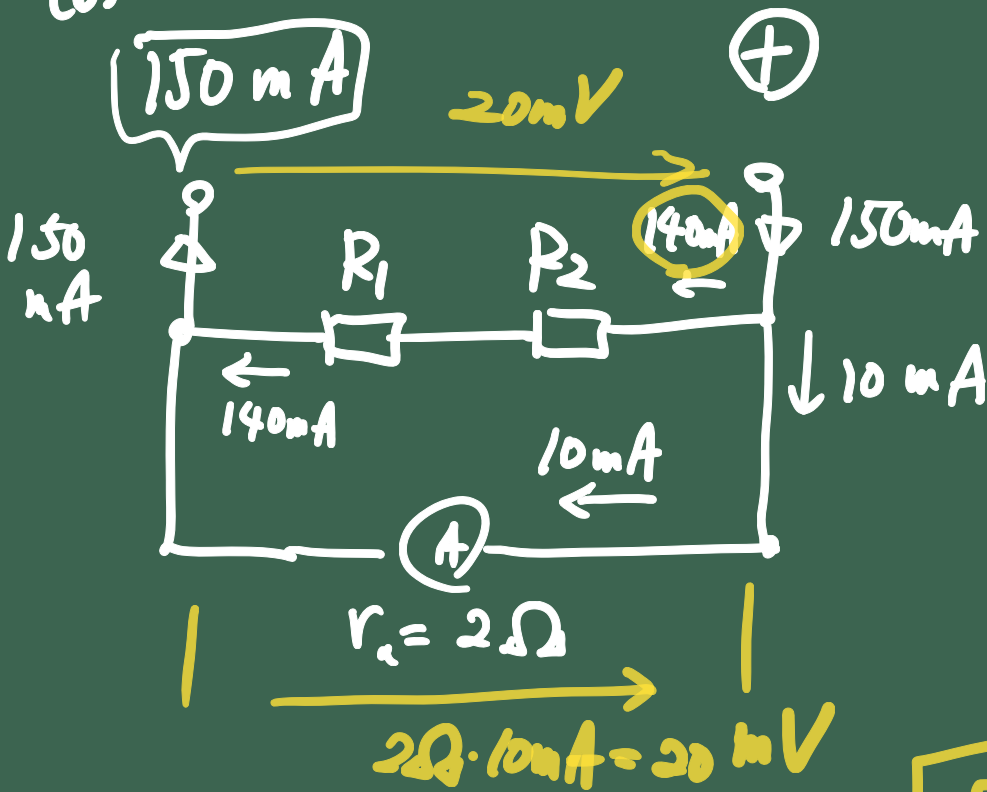

$$R_1 + R_2 = \frac{20 \text{ mV}}{140 \text{ mA}}$$

$$R_1 + R_2 = \frac{1}{7}$$

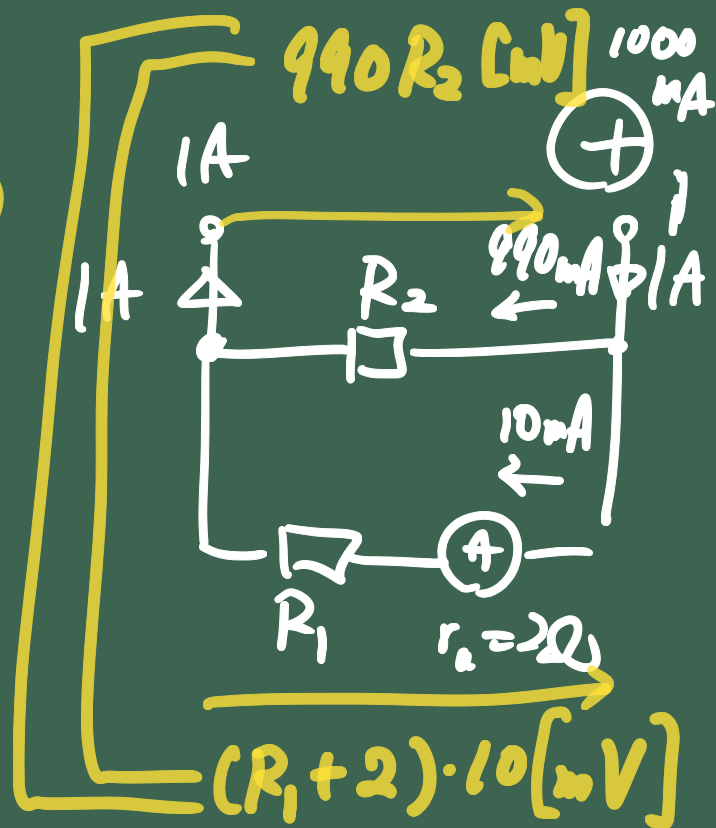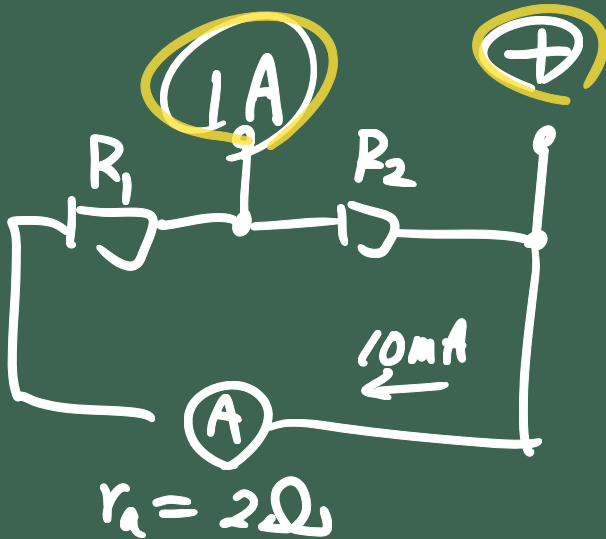

$$10(R_1 + 2) = 990 R_2$$

$$R_1 + 2 = 99 R_2$$

$$R_1 + R_2 = \frac{1}{7}$$

$$R_1 - 99R_2 = -2$$

---

$$100R_2 = \frac{1}{7} - (-2) = \frac{1+14}{7} = \frac{15}{7}$$

$$R_2 = \frac{15}{7 \times 100} = 0.0214 \text{ (}\Omega\text{)}$$

$$R_1 = \frac{1}{7} - R_2 = 0.121 \text{ (}\Omega\text{)}$$

























