
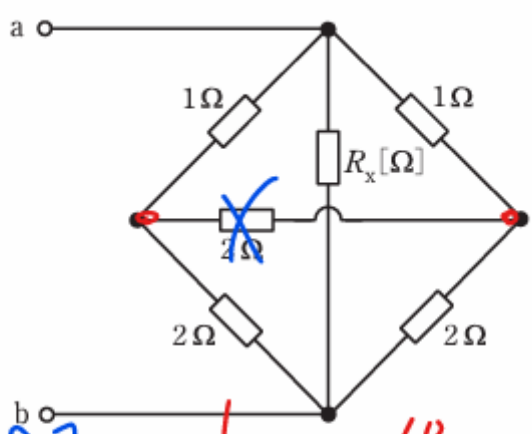
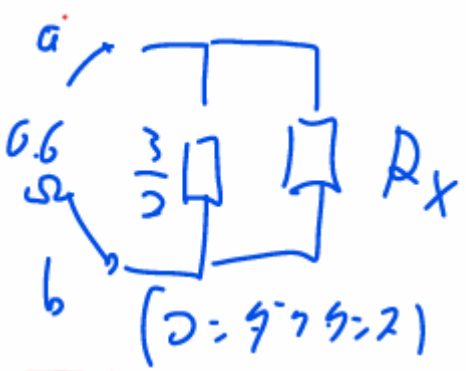


-1 C

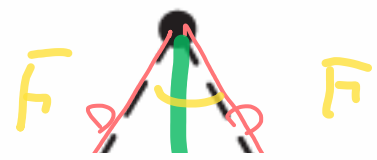

$$\frac{1}{R_x} + \frac{2}{3} = \frac{1}{0.6} \quad \text{CS} \quad = \frac{1}{6/10} = \frac{10}{6}$$

- (1) 1.0
- (2) 1.2
- (3) 1.5
- (4) 1.8
- (5) 2.0

(詞系平均)

1:2 4:3 式


$$ax + b = c$$

$$\frac{1}{x} = R_x$$

(1:2)



$$\frac{1}{R_x} = \frac{10}{63} - \frac{2}{3} = \frac{3}{5} = 1$$

$$R_x = 1$$

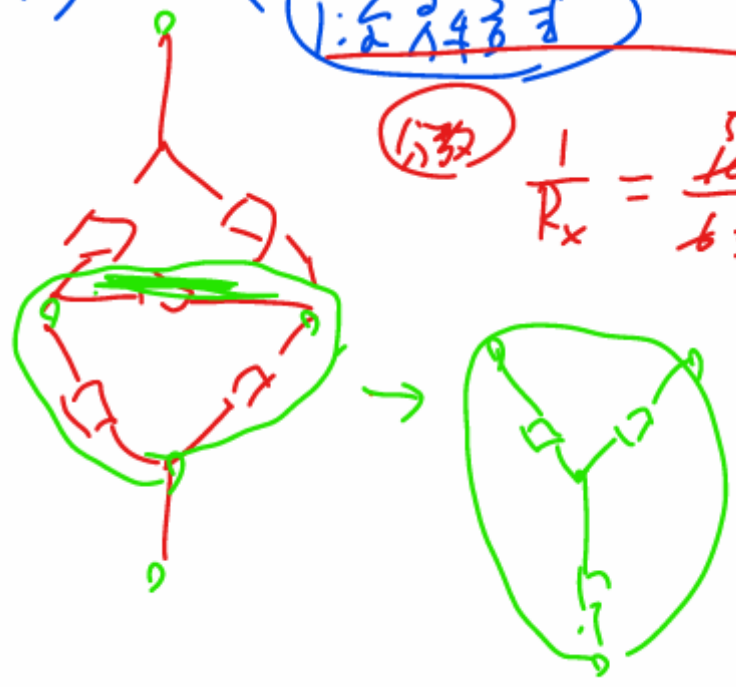


(F < 0 3/4)

$$|F| = \frac{1}{1^2} = R = F$$

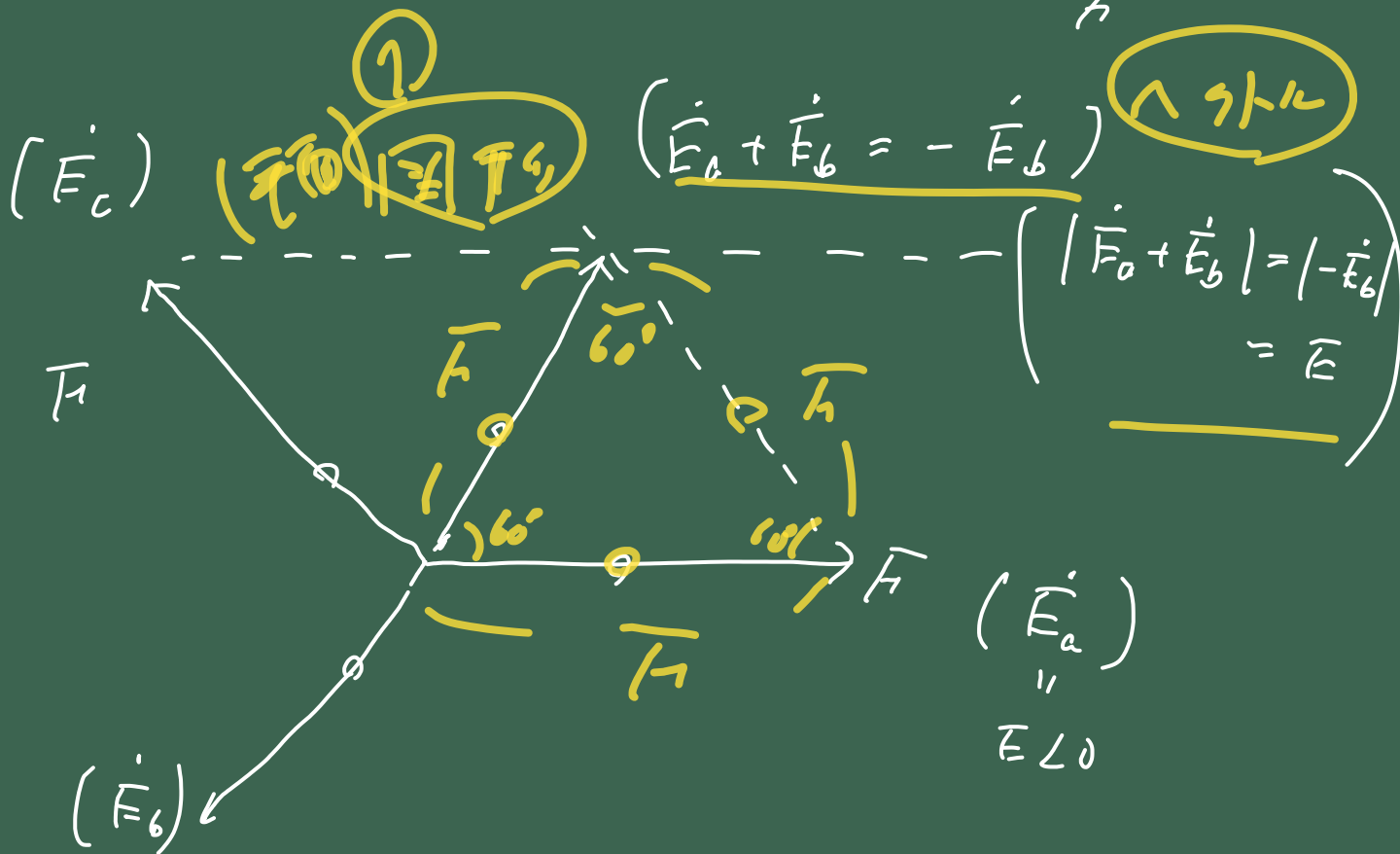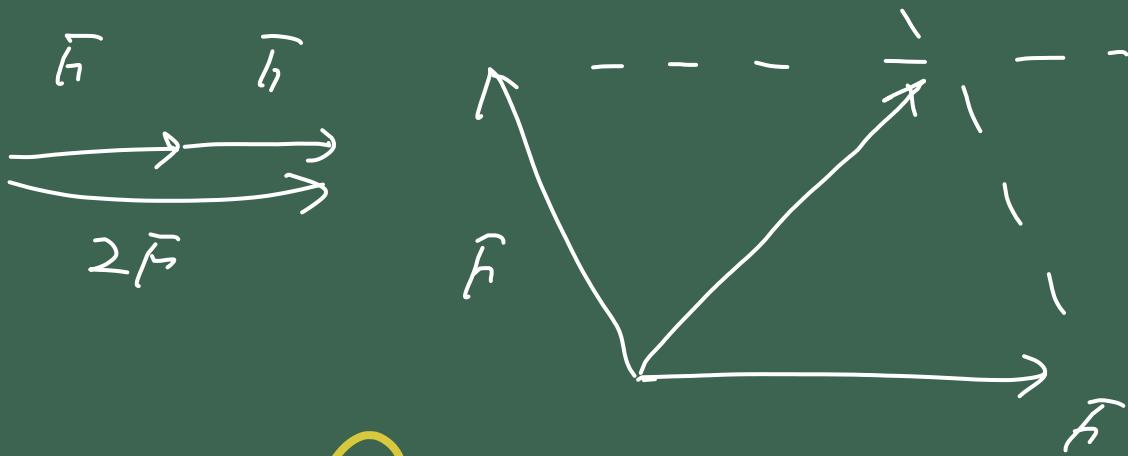

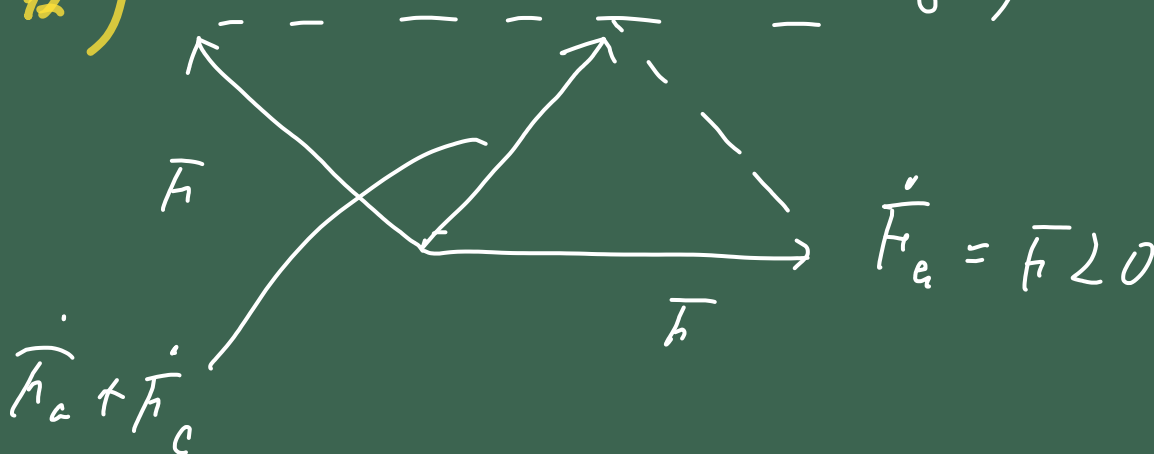(複素数) $\dot{E}_c = \bar{E} \angle \left(-\frac{4\pi}{3}\right) = \bar{E} \angle \left(\frac{2\pi}{3}\right)$




$$\begin{aligned} \vec{F}_a + \vec{F}_c &= F \angle 0 + F \angle \frac{2\pi}{3} \\ &= F + j0 + F \cos \frac{2\pi}{3} + j F \sin \frac{2\pi}{3} \\ &= F + \frac{1}{2} F + j \frac{\sqrt{3}}{2} F \end{aligned}$$

$$= \frac{3}{2} F + j \frac{\sqrt{3}}{2} F$$


$$|\vec{F}_a + \vec{F}_c| = \sqrt{\left(\frac{3}{2} F\right)^2 + \left(\frac{\sqrt{3}}{2} F\right)^2}$$

$$= \frac{F}{2} \sqrt{18 + 3}$$

$$= \frac{F}{2} \sqrt{21} = F$$

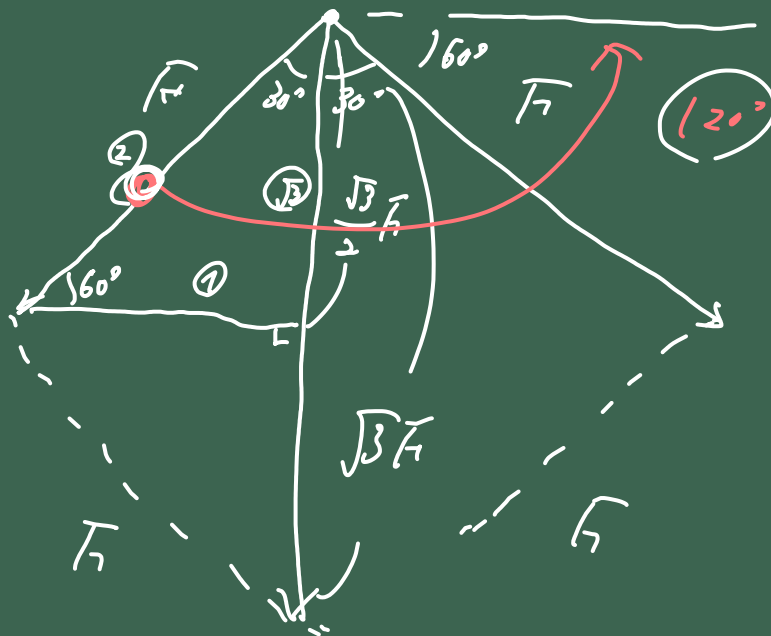

$$\vec{F}_2 = \sqrt{3} F$$

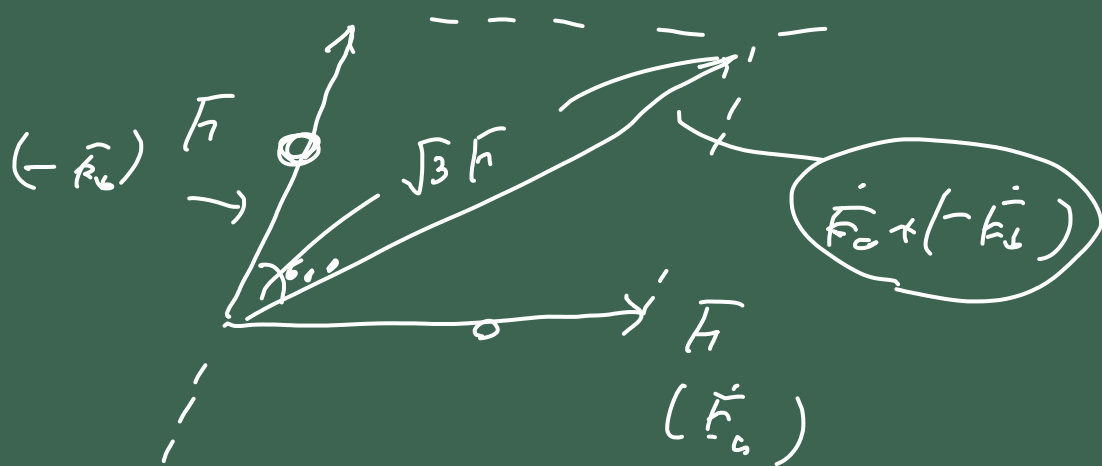

$$(\vec{F}_c) \quad \checkmark$$

$$\begin{aligned} \vec{F}_a + (-\vec{F}_b) &= F \angle 0 + F \angle \frac{\pi}{3} \\ &= F + j0 + F \cos \frac{\pi}{3} + j F \sin \frac{\pi}{3} \end{aligned}$$

$$= E + E \frac{1}{2} + j \frac{\sqrt{3}}{2} E$$

$$= \frac{3}{2} E + j \frac{\sqrt{3}}{2} E$$



$$|E_a + (-E_b)| = \sqrt{\left(\frac{3}{2} E\right)^2 + \left(\frac{\sqrt{3}}{2} E\right)^2}$$

$$= \frac{E}{2} \sqrt{3^2 + \sqrt{3}^2}$$

$$= \frac{E}{2} \sqrt{12}$$

$$= \frac{E}{2} \sqrt{4 \times 3} = \sqrt{3} E$$

~~✗~~

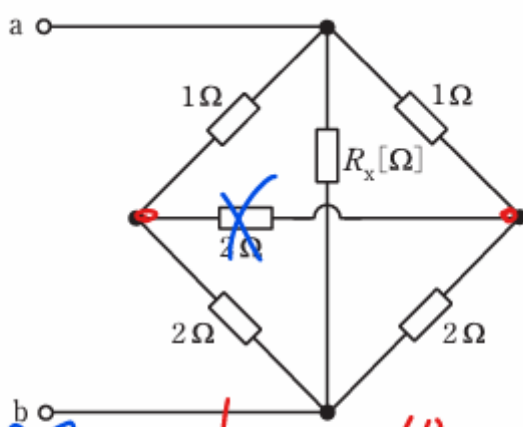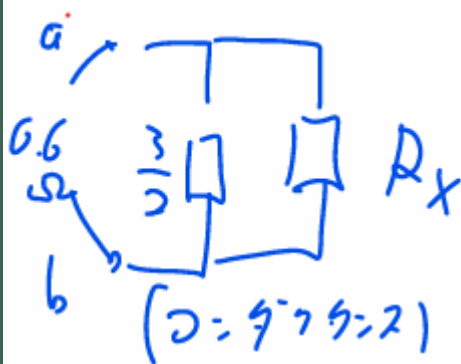

$$\frac{1}{R_x} + \frac{2}{3} = \frac{1}{0.6} \quad \text{CS} \quad = \frac{1}{6/10} = \frac{10}{6}$$

- (1) 1.0 (2) 1.2 (3) 1.5 (4) 1.8 (5) 2.0

(詞) 4. 7. 9. 2)


1: 2 4 3 5 $a x + b = c$

$$\frac{1}{x} = R_x$$


(1.7)

$$\frac{1}{R_x} = \frac{10}{63} - \frac{2}{3} = \frac{3}{3} = 1$$

$R_x = 1$

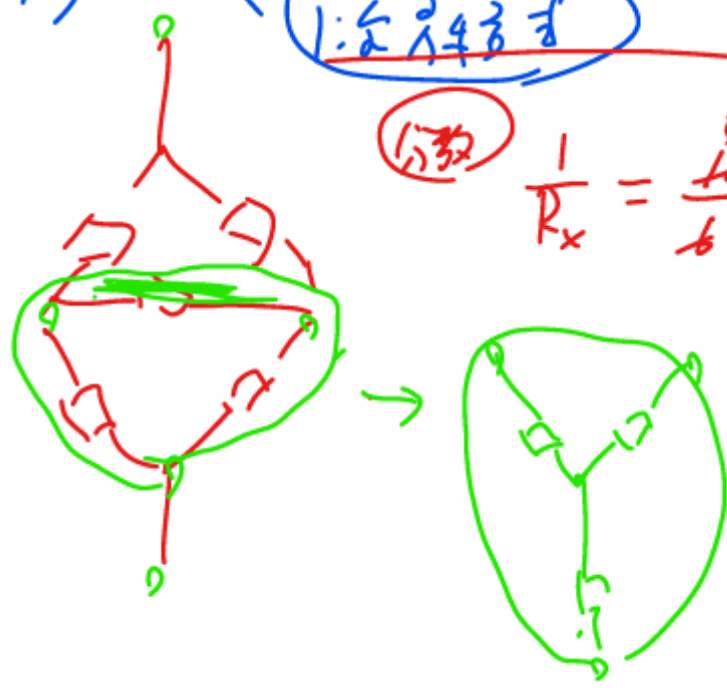

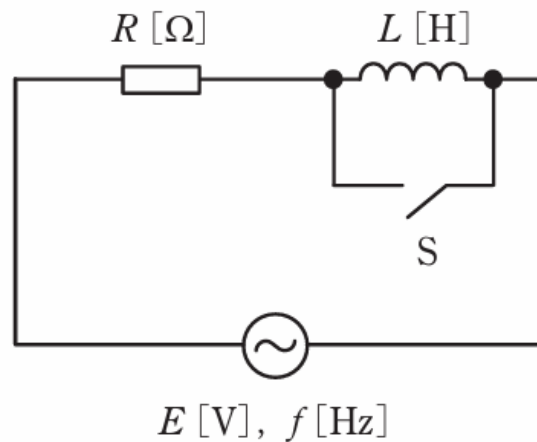問8 図のように、周波数 f [Hz] の正弦波交流電圧 E [V] の電源に、 R [Ω] の抵抗、インダクタンス L [H] のコイルとスイッチ S を接続した回路がある。スイッチ S が開いているときに回路が消費する電力[W]は、スイッチ S が閉じているときに回路が消費する電力[W]の $\frac{1}{2}$ になった。このとき、 L [H] の値を表す式として、正しいものを次の(1)～(5)のうちから一つ選べ。



共有の停止

(1) $2\pi f R$

(2) $\frac{R}{2\pi f}$

(3) $\frac{2\pi f}{R}$

(4) $\frac{(2\pi f)^2}{R}$

(5) $\frac{R}{\pi f}$

$2\pi f L$ [Ω]
 X_L

L [H] = $\frac{X_L}{2\pi f}$ [$\frac{\Omega}{\text{Hz}}$]

次元 単位

$$150\text{cm} + 50\text{kg} \quad \times$$

$$150\text{cm} + 2.2\text{m} \quad \circ$$

$$= 15\text{m} + 2.2\text{m} \quad \circ$$

$$= (15 + 2.2) \underset{\substack{| \\ 1\text{m}}}{\text{m}} = 37\text{m}$$

$$2\text{m} \times 4\text{m} = 8\text{m}^2$$

$$\frac{8\text{m}^2}{4\text{m}} = 2\text{m}$$

$$I = \frac{V}{R} \quad [A] = \left[\frac{V}{\Omega} \right]$$

$$\left(\frac{R}{\sqrt{R^2 + (\omega L)^2}}\right) I_{\text{OFF}} = \frac{E}{\sqrt{R^2 + (\omega L)^2}} \quad \textcircled{1} \quad 1 - \cos = 1$$

$$\left(\frac{1}{R}\right) I_{\text{ON}} = \frac{E}{R} \quad \textcircled{2} \quad \left(\frac{1}{\sqrt{2}}\right)$$

$$R I_{\text{OFF}}^2 \quad R I_{\text{ON}}^2 = 1 \cdot 2 \quad \left(\begin{array}{l} \star \text{ 単位} \\ \textcircled{3} \end{array} \right)$$

$$\frac{1}{R^2 + (\omega L)^2} \cdot \frac{1}{R^2} = 1 \cdot 2$$

$$R^2 + (\omega L)^2 \quad R^2 = 2 \quad 1$$

$$R^2 + (\omega L)^2 = 2R^2$$

$$R = \omega L$$

$$L = \frac{R}{\omega} = \frac{R}{2\pi f}$$

